

Logic Design using Modules


Gerhard Dueck

March 9, 2010

Outline

- 1 Logic Design using PLAs
- 2 PLAs with Input Decoders

PLA structure

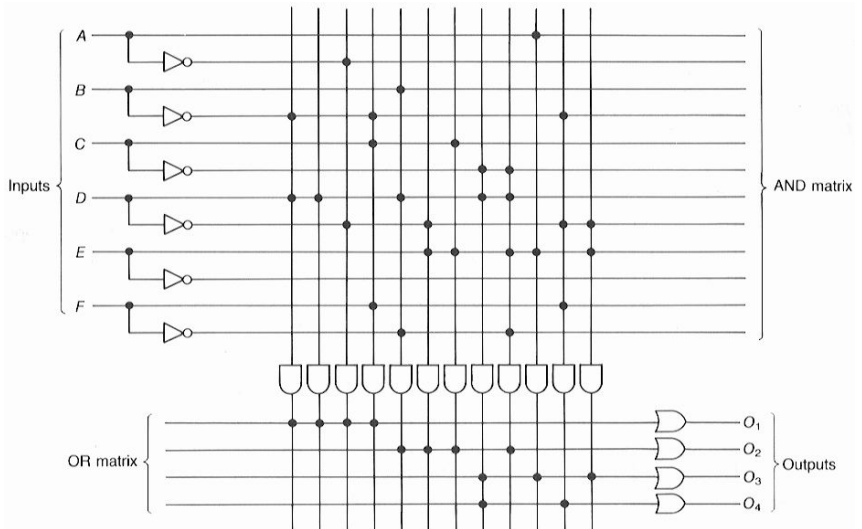

PLA

- Direct relation to SOP
- Logic design is easy
- Layouts are easy—PLAs are structured

Output Phase Optimization

Networks can often be simplified by realizing \bar{f} , the complement of f , instead of the original function f .

Definition (Achilles' heel function)

$f = x_1x_2x_3 \vee x_4x_5x_6 \vee x_7x_8x_9 \vee \dots \vee x_{n-2}x_{n-1}x_n$ ($n = 3r$) is an n -variable **Achilles' heel function**.

Lemma

Let f be an n -variable Achilles' heel function ($n = 3r$). Let $t(f)$ be the number of product terms in a MSOP for f . Then, $t(f) = r$, and $t(\bar{f}) = 3^r$.

The complexity for f and \bar{f} can be quite different.

Some Properties

Property (Function with low density)

For n -variable functions whose densities are r , if $r \leq 2^{n-1}$, then the average number of products in the SOPs increases as r increases.

Property (Function with high density)

For n -variable functions whose densities are greater than 2^{n-1} , the number of prime implicants is usually very large, and minimization is difficult. So, usually, the SOPs for the complements of the functions are simpler than the SOPs for the original functions.

Output Phase Optimization

Theorem

In a truth table for an n -input multiple-output function, if there are t input combinations that make all the output combinations 0, then the functions can be realized by a PLA with at most $(2^n - t)$ products.

From the properties and the theorem we have the following: A good output phase has

- large number of input combinations that will make all outputs 0's
- large number of 0's in the truth table.

An Example

Example (Output phase assignment)

Design a 4-input **bit counting circuit** (WGT4) (see next slide)

- The straightforward PLA realization requires 15 products.
- The complemented function has no zero rows.
- The optimized output phase has 10 products.

WGT4

Input				Output								
				Original			Optimized			Compl.		
x_1	x_2	x_3	x_4	f_2	f_1	f_0	f_2	f_1	f_0	f_2	f_1	f_0
0	0	0	0	0	0	0	0	1	0	1	1	1
0	0	0	1	0	0	1	0	1	1	1	1	0
0	0	1	0	0	0	1	0	1	1	1	1	0
0	0	1	1	0	1	0	0	0	0	1	0	1
0	1	0	0	0	0	1	0	1	1	1	1	0
0	1	0	1	0	1	0	0	0	0	1	0	1
0	1	1	0	0	1	0	0	0	0	1	0	1
0	1	1	1	0	1	1	0	0	1	1	0	0
1	0	0	0	0	0	1	0	1	1	1	1	0
1	0	0	1	0	1	0	0	0	0	1	0	1
1	0	1	0	0	1	0	0	0	0	1	0	1
1	0	1	1	0	1	1	0	0	1	1	0	0
1	1	0	0	0	1	0	0	0	0	1	0	1
1	1	0	1	0	1	1	0	0	1	1	0	0
1	1	1	0	0	1	1	0	0	1	1	0	1
1	1	1	1	1	0	0	1	1	0	0	1	1

Output Phase Optimization

The previous example leads to the following theorem:

Theorem

The minimum PLA for the n -input bit-counting circuit (WGTn, $n = 2r$ requires $(2^n - 1)$ products when the output phase is original, and $2^n - \binom{n}{n/2}$ products when the output phase is optimized.

Algorithm

Algorithm (Near optimum output phase assignment)

- 1 For a given m -output function let PLA1 (with $2m$ outputs) be the PLA that realizes all m outputs and their complements.
- 2 Let the output part of PLA1 be G . Attach the labels P_1, P_2, \dots, P_t to the rows of G . For each output $f_i (i = 0, \dots, m - 1)$, make an SOP: $L_i = P_{a_1} P_{a_2} \cdots P_{a_r} \vee P_{b_1} P_{b_2} \cdots P_{b_s}$ where $P_{a_1} P_{a_2} \cdots P_{a_r}$, denote the rows whose $(i + 1)$ th column of G are 1's (i.e. f_i). $P_{b_1} P_{b_2} \cdots P_{b_s}$, denote the rows whose $(i + m + 1)$ th column of G are 1's (i.e. \bar{f}_i).
- 3 Expand the expression $Q(P_1, P_2, \dots, P_t) = L_0 \cdot L_1 \cdots L_{m-1}$ into an SOP, and obtain the product with the fewest literals.
- 4 Obtain the output phase corresponding to the product obtained in 3.

Example: output phase assignment

Example 12.2 Let us obtain the output phase for a 4-input bit-counting circuit (WGT4), using Algorithm 12.1.

1. Table 12.1 is the truth table for $(f_2, f_1, f_0, \bar{f}_2, \bar{f}_1, \bar{f}_0)$. By simplifying this PLA by MINI2, we have a PLA shown in Table 12.2.
2. Let G be the output PLA1. Then,

f_2	f_1	f_0	\bar{f}_2	\bar{f}_1	\bar{f}_0	
1	0	0	0	1	1	P_1
0	0	1	0	1	0	P_2
0	0	1	0	1	0	P_3
0	0	1	0	1	0	P_4
0	0	0	0	1	1	P_5
0	0	1	0	1	0	P_6
0	1	1	0	0	0	P_7
0	1	0	0	0	1	P_8
0	1	0	0	0	1	P_9
0	1	0	0	0	1	P_{10}
0	1	0	0	0	1	P_{11}
0	1	1	0	0	0	P_{12}
0	1	0	0	0	1	P_{13}
0	1	0	1	0	1	P_{14}
0	1	1	1	0	0	P_{15}
0	1	1	1	0	0	P_{16}
0	0	0	1	0	0	P_{17}
0	0	0	1	0	0	P_{18}

Let L_2, L_1 , and L_0 be the expressions for outputs f_2, f_1 , and f_0 , respectively. Then, we have

$$L_2 = P_1 \vee P_{14} P_{15} P_{16} P_{17} P_{18},$$

$$L_1 = P_7 P_8 P_9 P_{10} P_{11} P_{12} P_{13} P_{14} P_{15} P_{16} \vee P_1 P_2 P_3 P_4 P_5 P_6, \text{ and}$$

$$L_0 = P_2 P_3 P_4 P_6 P_7 P_{12} P_{15} P_{16} \vee P_1 P_5 P_8 P_9 P_{10} P_{11} P_{13} P_{14}.$$

Example: output phase assignment

Table 12.2 WGT4 simplified by MINI2.

Input part				Output part
x_4	x_3	x_2	x_1	
01	01	01	01	100011
01	10	10	10	001010
10	10	10	01	001010
10	10	01	10	001010
10	10	10	10	000011
10	01	10	10	001010
01	10	01	01	011000
01	10	10	01	010001
01	10	01	10	010001
10	10	01	01	010001
10	01	01	10	010001
10	01	01	01	011000
10	01	10	01	010001
01	01	10	10	010101
01	01	01	10	011100
01	01	10	01	011100
10	11	11	11	000100
11	10	11	11	000100

Example: output phase assignment

3. By expanding the logical expression $Q(P_1, P_2, \dots, P_{18}) = L_0 \cdot L_1 \cdot L_2$, we have the following expression:

$$P_1 P_2 P_3 P_4 P_5 P_6 P_8 P_9 P_{10} P_{11} P_{13} P_{14} P_{15} P_{16} P_{17} P_{18}$$

$$\vee P_1 P_2 P_3 P_4 P_5 P_6 P_7 P_{12} P_{14} P_{15} P_{16} P_{17} P_{18}$$

$$\vee P_1 P_5 P_7 P_8 P_9 P_{10} P_{11} P_{12} P_{13} P_{14} P_{15} P_{16} P_{17} P_{18}$$

$$\vee P_2 P_3 P_4 P_6 P_7 P_8 P_9 P_{10} P_{11} P_{12} P_{13} P_{14} P_{15} P_{16} P_{17} P_{18}$$

$$\vee P_1 P_2 P_3 P_4 P_5 P_6 P_8 P_9 P_{10} P_{11} P_{13} P_{14}$$


$$\vee P_1 P_2 P_3 P_4 P_5 P_6 P_7 P_{12} P_{15} P_{16}$$

$$\vee P_1 P_5 P_7 P_8 P_9 P_{10} P_{11} P_{12} P_{13} P_{14} P_{15} P_{16}$$

$$\vee P_1 P_2 P_3 P_4 P_6 P_7 P_8 P_9 P_{10} P_{11} P_{12} P_{13} P_{14} P_{15} P_{16}$$

Note that the first product corresponds to $(\bar{f}_2, \bar{f}_1, \bar{f}_0)$, the second one corresponds to $(\bar{f}_2, \bar{f}_1, f_0)$, ..., and the last term corresponds to (f_2, f_1, f_0) . The product with the fewest literals is the 6-th, and it corresponds to the output (f_2, \bar{f}_1, f_0) . ■

PLAs with Input Decoders

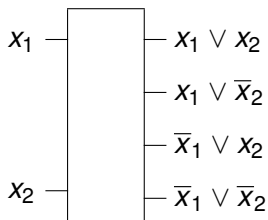

- Standard PLAs have 1-bit input decoders.
- The decoders for PLAs with 2-bit input decoders are shown on the left.
- How many 2 input decoders are possible?

Principle of PLAs with input decoders

- 2-bit input decoders realize all maxterms of two variables.
- An two input function can be realized by a logical product of these maxterms.
- This is the canonical expression

$$f(x_1, x_2) = (c_0 \vee x_1 \vee x_2)(c_1 \vee x_1 \vee \bar{x}_2)(c_2 \vee \bar{x}_1 \vee x_2)(c_3 \vee \bar{x}_1 \vee \bar{x}_2)$$

- What is the worst case for 2-variable function using a standard PLA?

Coincidence function

Example (Coincidence)

Consider the $f = f_1(x_1, x_2)f_2(x_3, x_4)f_3(x_5, x_6)$, where

$$f_1(x_1, x_2) = x_1x_2 \vee \bar{x}_1\bar{x}_2$$

$$f_2(x_3, x_4) = x_3x_4 \vee \bar{x}_3\bar{x}_4, \text{ and}$$

$$f_3(x_5, x_6) = x_5x_6 \vee \bar{x}_5\bar{x}_6$$

Show the PLA realization (see Fig. 12.7 in the text).

Representation for PLAs with input decoders

- 2 variables can be combined into one 4-valued variable.
- In the coincidence example, let $X_1 = (x_1, x_2)$, $X_2 = (x_3, x_4)$, and $X_3 = (x_5, x_6)$.
- The function is represented as

X_1				X_2				X_3					
00	01	10	11	00	01	10	11	00	01	10	11		
1	0	0	1	-	1	0	0	1	-	1	0	0	1

Theorem

- 1 Each product line in a PLA with 2-bit input decoders realizes a product

$$f_1(x_1, x_2)f_2(x_3, x_4) \cdots f_r(x_{n-1}, x_n)$$

- 2 The function realized by the product lines is represented by

$$c_0^1 c_1^1 c_2^1 c_3^1 - c_0^2 c_2^2 c_2^2 c_3^2 - \cdots - c_0^r c_r^r c_2^r c_3^r (n = 2r)$$

Design method for PLAs with input decoders

Algorithm (Design with input decoders)

Step 1 Transform the logical expression into a bit representation

- 1 Partition input variables into pairs.
- 2 Derived bit representation for the function with 4-valued variables.

Step 2 Transform the bit representation into a PLA.

- 1 Input part: For the part 0, make an AND connection
- 2 Output part: For the part 1, make an OR connection

Example (2-bit adder)

Example (2-bit adder)

Find the bit representation for the 2 bit adder.

$(x_1, x_0) + (y_1, y_0) = (z_2, z_1, z_0)$. We have:

$$z_0 = x_0 \oplus y_0 = x_0 \bar{y}_0 \vee \bar{x}_0 y_0,$$

$$z_1 = x_0 y_0 \oplus x_1 \oplus y_1$$

$$= (\bar{x}_0 \vee \bar{y}_0)(x_1 \bar{y}_1 \vee \bar{x}_1 y_1) \vee (x_0 y_0)(x_1 y_1 \vee \bar{x}_1 \bar{y}_1), \text{ and}$$

$$z_2 = x_1 y_1 \vee (x_0 y_0)(x_1 \vee y_1).$$

Example (2-bit adder) cont.

Example (2-bit adder (cont.))

Let $X_1 = (x_0, y_0)$, $X_2 = (x_1, y_1)$, and $X_3 = (z_0, z_1, z_2)$. Then we have

X_1	-	X_2	-	X_3
0110	-	1111	-	100
1110	-	0110	-	010
0001	-	1001	-	010
1111	-	0001	-	001
0001	-	0111	-	001

The PLA realization is shown in Fig. 12.8 (text)

Bound for an arbitrary function

Theorem

An arbitrary n -variable function ($n = 2r$) is realized by a PLA with 2-bit input decoders using at most 2^{n-2} products.

Proof.

An arbitrary n -variable function is expanded as

$$f = \bigvee_a f(x_1, x_2, a) \cdot (x_3^{a_3} x_4^{a_4}) \cdot (x_5^{a_5} x_6^{a_6}) \cdot \dots \cdot (x_{n-1}^{a_{n-1}} x_n^{a_n}),$$

where $a = (a_3, a_4, \dots, a_n)$, $a_i \in \{0, 1\}$. The number of product terms is 2^{n-2} . □

Bound for symmetric functions

Theorem

An arbitrary n -variable symmetric function ($n = 2r$) is realized by a PLA with 2-bit input decoders using at most 3^{r-1} products.

Proof.

An arbitrary n -variable symmetric function is expanded as

$$f = \bigvee_b S(x_1, x_2, b) \cdot S_{b_2}(x_3, x_4) \cdot S_{b_3}(x_5, x_6) \cdot \cdots \cdot S_{b_r}(x_{n-1}, x_n),$$

where $b = (b_2, b_3, \dots, b_r)$, $b_i \in \{0, 1, 2\}$, and

$$S_j(x_i, x_{i+1}) = \begin{cases} 1, & \text{when } x_i + x_{i+1} = j \\ 0, & \text{otherwise} \end{cases}$$

Note that $S(x_1, x_2, b)$ is symmetric with respect to x_1 and x_2 . □

Bound for parity functions

Theorem

An n -variable parity function ($n = 2r$) is realized by a PLA with 2-bit input decoders using at most 2^{r-1} products.

Proof.

An n -variable parity function is expanded as

$$f = \bigvee_c P(x_1, x_2, c) \cdot P_{c_2}(x_3, x_4) \cdot P_{c_3}(x_5, x_6) \cdot \cdots \cdot P_{c_r}(x_{n-1}, x_n),$$

where $c = (c_2, c_3, \dots, c_r)$, $c_i \in \{0, 1\}$, and

$$P_{c_j}(x_i, x_{i+1}) = x_i \oplus x_{i+1} \oplus c_j$$

Note that $P(x_1, x_2, c)$ is also a parity function. □

Comparison

Table: Number of products to realize n -variable functions.

	1-bit decoders	2-bit decoders
Arbitrary function (worst case)	2^{n-1}	2^{n-2}
Symmetric function (worst case)	2^{n-1}	$(\sqrt{3})^{n-2}$
Parity function	2^{n-1}	$(\sqrt{2})^{n-2}$
Adder	$6 \cdot 2^n - 4n - 5$	$n^2 + 1$
10-variable random function (average)	163	120

Assignment of input variables

Example

Given a 2-bit adder

- 5 products are needed with assignment $X_1 = (x_0, y_0)$ and $X_2 = (x_1, y_1)$.
 - 9 products are needed with assignment $X_1 = (x_0, x_1)$ and $X_2 = (y_0, y_1)$.
-
- number of product terms greatly depends on the variable assignment
 - **Optimum assignment of input variables**
 - exhaustive (how many possibilities?)
 - for experimental results see Table 12.3
 - heuristics

Optimum assignment

Definition (Partition)

Let $I = \{1, 2, \dots, n\}$ be a set of subscripts for the input variables X . Let Π be a partition of I . Let $t(f : \Pi)$ be the number of products in a MSOP for f , under the partition Π . Let F be an SOP for the function f . Let $q(i, j)$ be the number of different products in the SOP that are obtained from F by deleting literals for x_i and x_j . Let $t(f : \Pi_{ij})$ be the number of products in a minimum SOP for f , when x_i and x_j are paired.

Optimum assignment

Example

Let F be

$$F = \bar{x}_1\bar{x}_2x_3x_4 + \bar{x}_1x_2x_3x_4 + x_1\bar{x}_2\bar{x}_3x_4 + \\ x_1\bar{x}_2\bar{x}_3\bar{x}_4 + x_1\bar{x}_2x_3\bar{x}_4 + x_1x_2\bar{x}_3\bar{x}_4$$

$$q(1, 2) =$$

$$q(1, 3) =$$

$$q(1, 4) =$$

$$q(2, 3) =$$

$$q(2, 4) =$$

$$q(3, 4) =$$

Optimum assignment

Lemma

Let $\Pi_{ij} = \{[1], [2], \dots, [i, j], \dots, [n]\}$. Then, $t(f : \Pi_{ij}) \leq q(i, j)$.

Optimum assignment

Proof.

Let F be an SOP for f . Assume $i = 1$ and $j = 2$ (WLOG).

$$F = \bigvee_S x_1^{S_1} x_2^{S_2} \cdots x_n^{S_n}$$

where $S = (S_1, S_2, \dots, S_n)$, and $S_j \subseteq \{0, 1\}$. Note that

$$x_i^{S_i} = \begin{cases} 1, & \text{when } S_i = \{0, 1\} \\ x_i, & \text{when } S_i = \{1\} \\ \bar{x}_i, & \text{when } S_i = \{0\} \end{cases}$$

Factoring F by $x_1^{S_1} x_2^{S_2} \cdots x_n^{S_n}$ we have

$$F = \bigvee_{S^*} G(x_1, x_2, S^*) x_3^{S_3} x_4^{S_4} \cdots x_n^{S_n},$$

Optimum assignment

continued.

where $S^* = (S_3, S_4, \dots, S_n)$, and $S_i \subseteq \{0, 1\}$

- $t(F_1)$ is equal to the distinct number of patterns in $x_3^{S_3} x_4^{S_4} \dots x_n^{S_n}$.
- These are obtained from F by deleting literals x_1 and x_2
- $t(F_1) = q(1, 2)$ (by definition)
- Let $X_1 = (x_1, x_2)$. Replace $G(x_1, x_2, S^*)$ with literal $X_1^{T_1}$, ($T_1 \subseteq \{00, 01, 10, 11\}$) we have F_1 which is an SOP under partition Π_{ij} .
- $t(f : \Pi_{ij}) \leq t(F_1)$
- Thus we have $t(f : \Pi_{ij}) \leq q(i, j)$



Variable assignment graph

Definition (Variable assignment graph)

A **variable assignment graph** G of an n -variable function $f(x_1, x_2, \dots, x_n)$ is a complete graph with weights satisfying the following conditions:

- 1 G has n nodes.
- 2 The weight of the edge (i, j) is $q(i, j)$.

Variable assignment

Algorithm (Assignment of variables for a PLA with 2-bit input decoders)

- 1 Obtain a (near) minimal SOP for f .
 - 2 Obtain a variable assignment graph G for f .
 - 3 Cover all nodes of G by a set of edges that have no common elements. Find a set such that the sum of the weights are minimum.
 - 4 Obtain the partition of the variables corresponding to the edges.
- The algorithm is heuristic. Minimal results are not guaranteed.
 - Experimental results show that it obtains optimal solutions for many functions.

Benchmarks

		Stand. PLA		PLA inp. decod.	
		Output phase		Output phase	
func.	products	Org.	Opt.	Org.	Opt.
addr4	255	75	61	17	14
inc8	255	37	36	21	20
log8	255	123	111	93	89
mul8	225	119	108	85	74
rdm8	255	76	76	47	47